

EECT 7325

PROJECT #2: 4*4 Bit Multiplier

Name: YI CHIEN CHIANG

UTD ID: 2021477769


Table of Contents

I.	Introduction.....	3
II.	2 Bit Full Adder.....	3
III.	4 Bit Full Adder.....	5
IV.	4*4 Bit Multiplier.....	7
V.	Simulation and Testing Table.....	10
VI.	Tradeoffs.....	12
VII.	Conclusion.....	12
VIII.	Reference.....	12

I. Introduction

The project 2 indicates to design the layout manually by using the cells we designed in the project 1 and do any type of design. Moreover, the size of the layout is probably about 100 cells. After the design, the correct simulation result is necessary and LVS and DRC result of the final layout should show no error. I chose a 4*4 bit multiplier for my topic and it was composed of 2 bits full adder and 4 bits full adder. The total layout are about 140 cells.

II. 2 Bit Full Adder

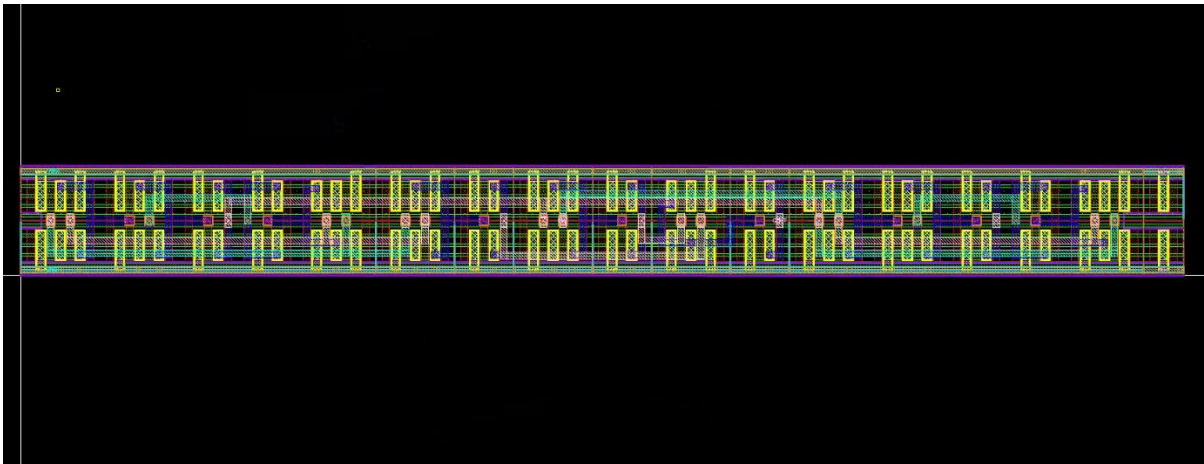Layout				
				
Fig 1-1. 2Bit Full Adder layout				
Template Table				
PMOS Width	NMOS Width	Cell Height	Cell Width	Cell Area
0.081um(3 Fins)	0.081um(3 Fins)	0.288um	3.078um	0.89um ²
Total Cells				
8 (2 XOR+ 2 NAND + 1NOR +3 Inverter)				

Schematic & Simulation

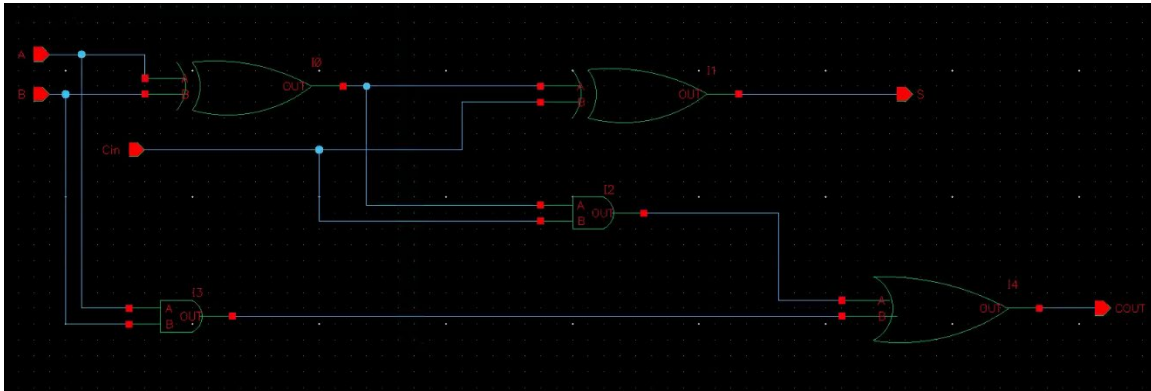


Fig 1-2. 2 Bit Full Adder Schematic

 
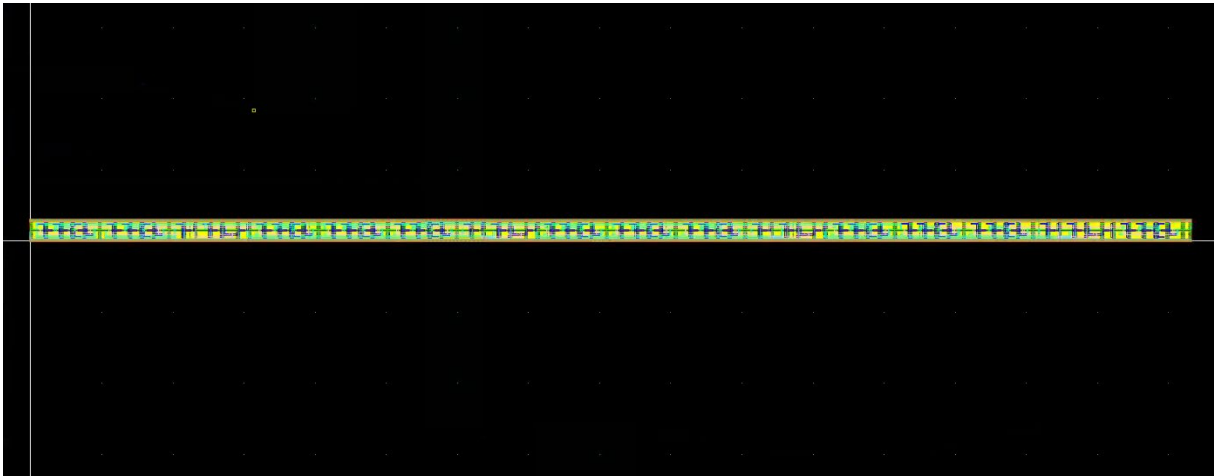


Fig 1-3. 2 Bit Full Adder Simulation

Testing Table

	TEST 1	TEST 2	TEST 3	TEST 4
Input	A : 0 B : 1	A : 0 B : 0	A : 1 B : 0	A : 1 B : 1
Value	1	0	1	2
Output	Sum:1 Cout:0	Sum:0 Cout:0	Sum:1 Cout:0	Sum:0 Cout:1

III. 4 Bit Full Adder

Layout				
				
Fig 2-1. 4 Bit Full Adder Layout				
Template Table				
PMOS Width	NMOS Width	Cell Height	Cell Width	Cell Area
0.081um(3 Fins)	0.081um(3 Fins)	0.288um	16.2um	4.66um ²
Total Cells				
36 (4 XOR + 4 2bits full adder)				

Schematic & Simulation

 


Fig 2-2. 4 Bit Full Adder Schematic

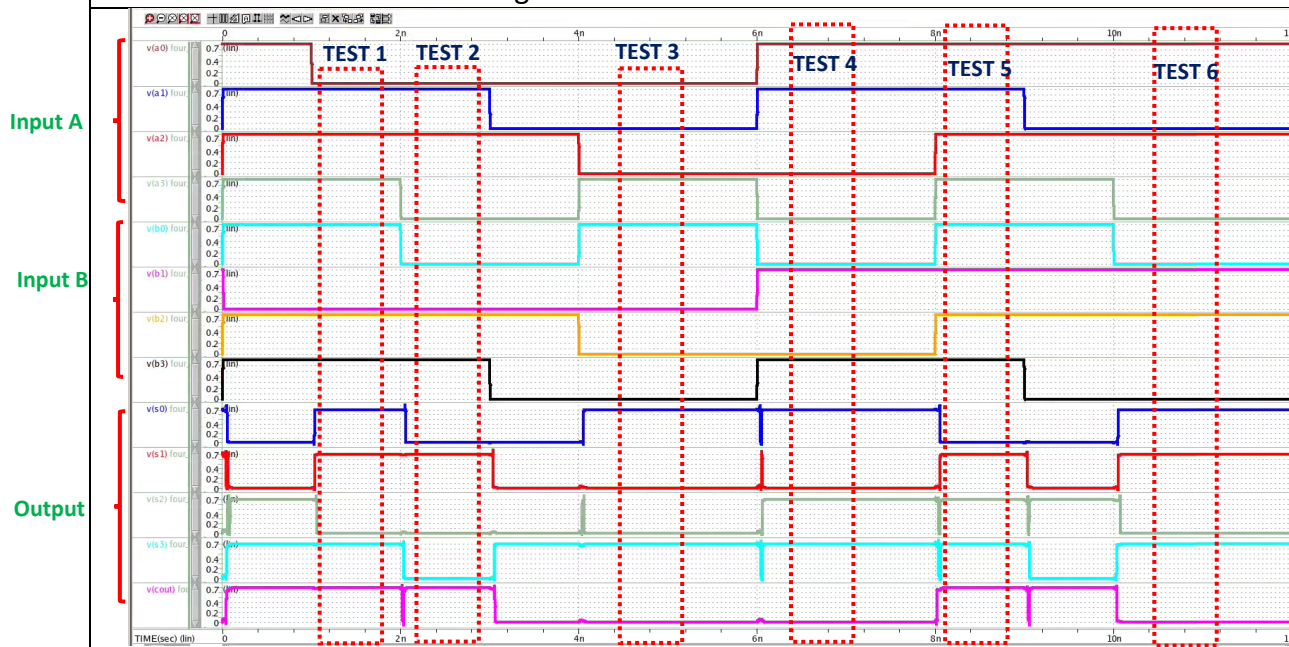


Fig 2-3. 4 Bit Full Adder Simulation

Testing Table

	TEST 1	TEST 2	TEST 3	TEST 4	TEST 5	TEST 6
Input	A : 1110 B : 1101	A : 0110 B : 1100	A : 1000 B : 0001	A : 0011 B : 1010	A : 1111 B : 1111	A : 0101 B : 0110
Value	$14+13 = 27$	$6+12 = 18$	$8+1 = 9$	$3+10 = 13$	$15+15 = 30$	$5+6 = 11$
Output	1011,Cout=1 =11+16= 27	0010,Cout=1 =2+16=18	1001,Cout=0 =9	1101,Cout=0 =13	1110,Cout=1 =14+16=30	1011,Cout=0 =11

IV. 4*4 Bit Multiplier

Layout

 


Fig 3-1. 4*4 Bit Multiplier layout

 


Fig 3-2. Part 1 of Multiplier – First 4 Bits Full adder

 


Fig 3-3. Part 2 of Multiplier – Second 4 Bits Full adder

 


Fig 3-4. Part 3 of Multiplier – Third 4Bits Full adder

 


Fig 3-5. Part 4 of Multiplier – And Gate

Template Table				
PMOS Width	NMOS Width	Cell Height	Cell Width	Cell Area
0.081um(3 Fins)	0.081um(3 Fins)	0.529um	54.648um	30um ²
Total Cells				
140 (3 4Bits Full Adder + 16 NAND +16 Inverter)				

DRC & LVS Match



Fig 3-6. Multiplier DRC

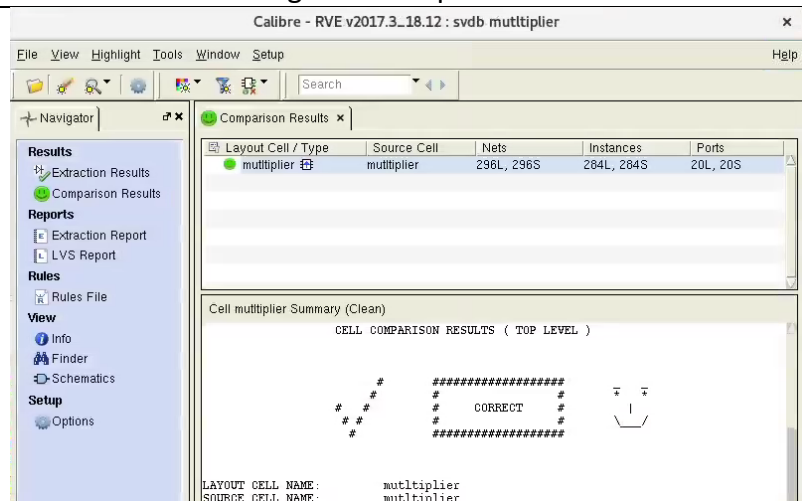


Fig 3-7. Multiplier LVS

Schematic


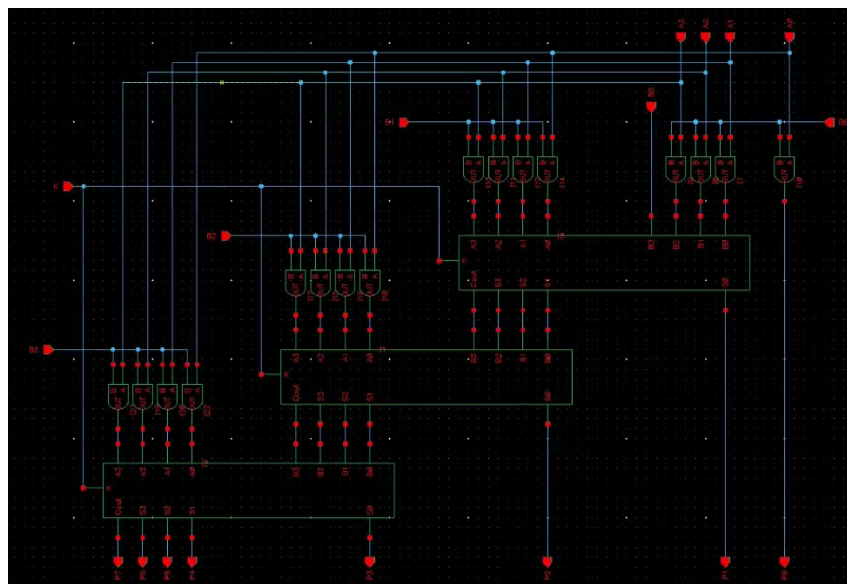


Fig 3-8. 4*4 Bit Multiplier Schematic

V. Simulation and Testing Table

 

Testing Table																	
K	BG	A0	A1	A2	A3	B0	B1	B2	B3	P0	P1	P2	P3	P4	P5	P6	P7
Cin	0	2 ⁰	2 ¹	2 ²	2 ³	2 ⁰	2 ¹	2 ²	2 ³	2 ⁰	2 ¹	2 ²	2 ³	2 ⁴	2 ⁵	2 ⁶	2 ⁷
		TEST 1			TEST 2			TEST 3		TEST 4			TEST 5		TEST 6		
Input		A : 1110 B : 1101			A : 1100 B : 1100			A : 0010 B : 0001		A : 1001 B : 0110			A : 0111 B : 1011		A : 0101 B : 1010		
Value		14*13 = 182			12*12 = 144			2*1 = 2		9*6 = 54			7*11 = 77		5*10 = 50		
Output		1011 0110 = 182			1001 0000 = 144			0000 0010 = 2		0011 0110 = 54			0100 1101 = 77		0011 0010 = 50		

 


Fig 3-10. 4*4 Bit Multiplier Simulation Result

Testing Table

Input	1111 + 1111
Value	15*15 =225
Output	1110 0001 =225

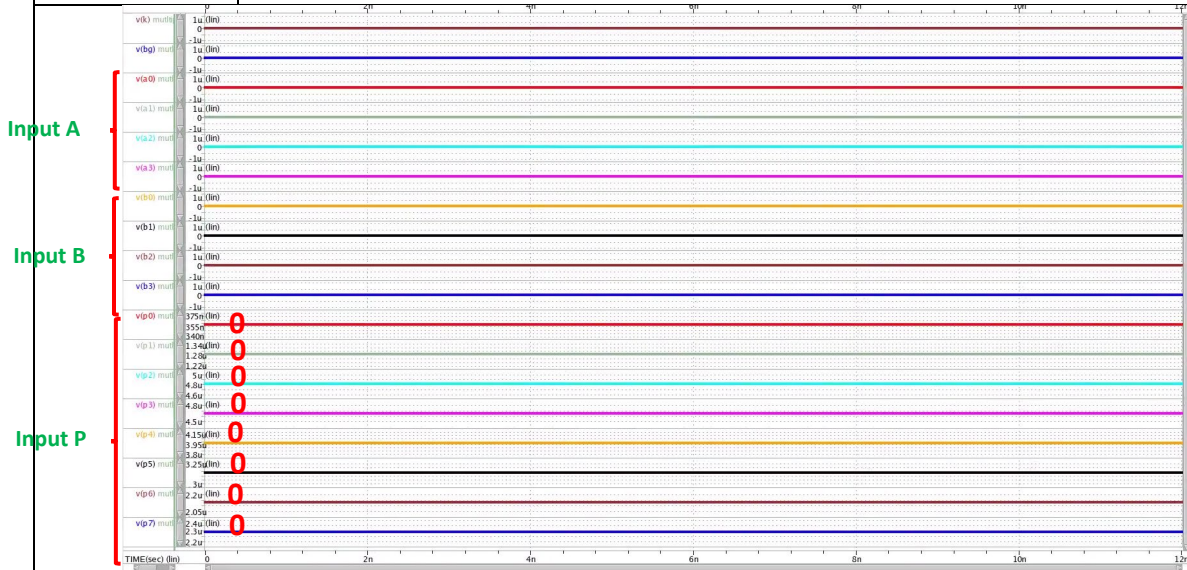


Fig 3-11. 4*4 Bit Multiplier Simulation Result

Testing Table

Input	0000 * 0000
Value	0*0 =0
Output	0000 0000 = 0

VI. Tradeoffs

The 4*4 multiplier can give product of 8-bit size by using the input number of 4-bit size. The maximum of the number is $15*15 = 225$. This multiplier is Combinational Multiplier. It performs multiplication of two unsigned binary numbers and the advantage is that it can generate intermediate products easily. The disadvantage is that it needs more layout area.

VII. Conclusion

The final project needs to design a larger and complicated layout system than before. I learned how to place the metal wiring in less space to decrease the layout area. After completing the layout design, LVS match was big challenge because the layout was large. I must check the total layout many times to reduce the mismatch to the schematic. I am glad that I can learn much more simulation skills and use the knowledge what I learn in this class when I do this project.

VIII. Reference

- Class Note
- Asap7_tutorial word file